

國立清華大學
超大型積體電路設計 VLSI Design



國立清華大學
NATIONAL TSING HUA UNIVERSITY

Homework 5

學號:111063548

姓名:蕭方凱

目錄

1. Please design a 4 bit binary synchronous up counter with clock frequency CLK = 200MHz, VDD = 1.8V (default) , VSS = 0V. You can use any architecture to complete the design. Try to minimize the power consumption of the counter. You can adjust the value of VDD for minimizing the power meanwhile the counter works correctly, and the maximum glitch should be less than 80ps.....	3
(a) Please describe how you design the counter and how to reduce the glitch and power consumption of counter.....	3
Counter Design	3
Glitch and power consumption reducing way	6
(b) Please list the glitch in each number (0 ~ 15) and find the maximum glitch.....	7
(c) Please measure the power of the counter.	7
2. Please design a 3 bit pseudo-random-bit-sequence (PRBS) generator with Linear Feedback Shift Register (LFSR) with clock frequency CLK = 200MHz, VDD = 1.8V, VSS = 0V. Try to minimize the power consumption of the PRBS generator.	8
(a) Please describe how you design the PRBS generator and show the pseudo-random sequence result to prove your design.	8
PRBS Design.....	8
The way to minimize the power.....	10
(b) Please measure the power of the PRBS generator.	11

1. Please design a 4 bit binary synchronous up counter with clock frequency CLK = 200MHz, VDD = 1.8V (default) , VSS = 0V. You can use any architecture to complete the design. Try to minimize the power consumption of the counter. You can adjust the value of VDD for minimizing the power meanwhile the counter works correctly, **and the maximum glitch should be less than 80ps.**
- (a) Please describe how you design the counter and how to reduce the glitch and power consumption of counter.

Counter Design

設計想法：

將一個一次只加 1 的電路(incrementer)與暫存器電路結合，即可實現 counter 計數器功能。概念圖如左下，其增值表如右下。

 



圖 1 synchronous counter

I ₃	I ₂	I ₁	I ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	1	1	0	0
1	1	0	0	1	1	0	1
1	1	0	1	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	0	0	0

圖 2 synchronous counter truth table

實際設計電路:

 參考講義上的 synchronous counter，本次作業以下圖為實際設計電路。



此電路組成，左邊為 half adder，提供 carry bit 和 sum bit，右邊則為 D Flip-Flop，提供暫存功能，每個 Flip-Flop 一次暫存 1 bit。

Schematic :

左下圖為 4 bits synchronous up counter，其中 DFF 沿用上次作業的設計，half adder 為右上圖，half adder 內部的 XOR gate 則為左下圖。

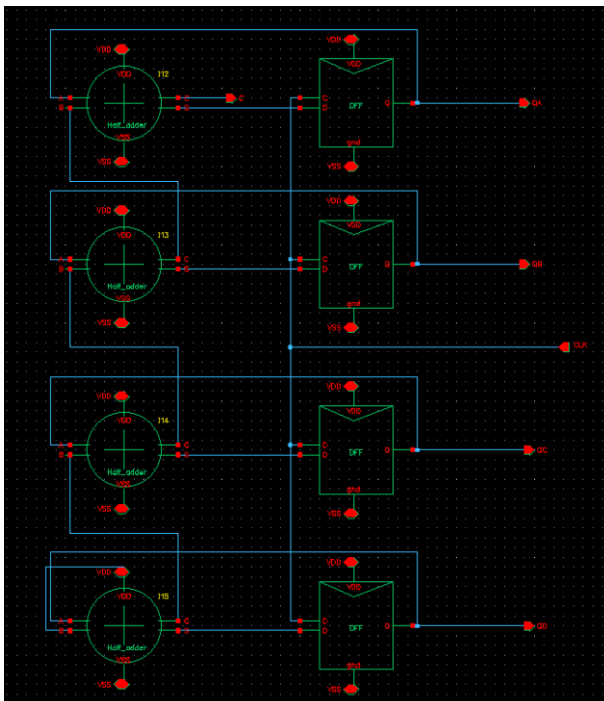


圖 3 4 bits synchronous up counter

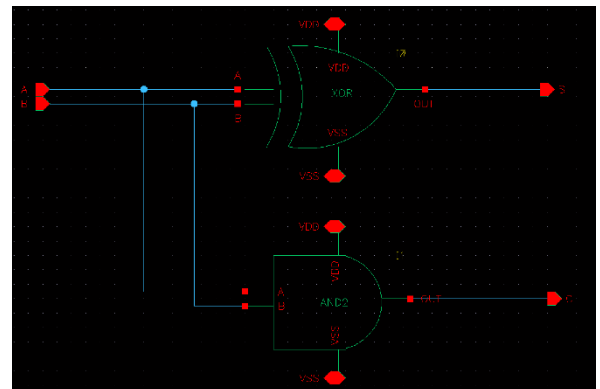


圖 4 half adder

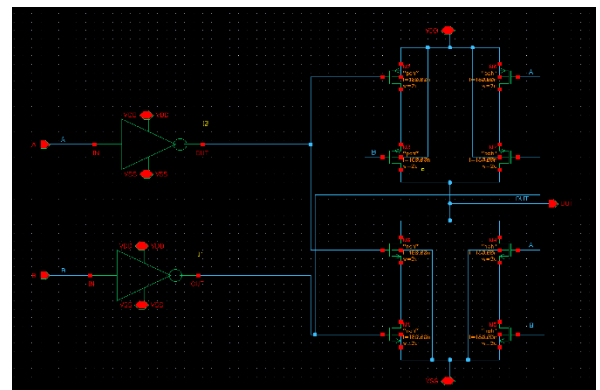


圖 5 XOR gate

設計完成後，模擬結果如下：

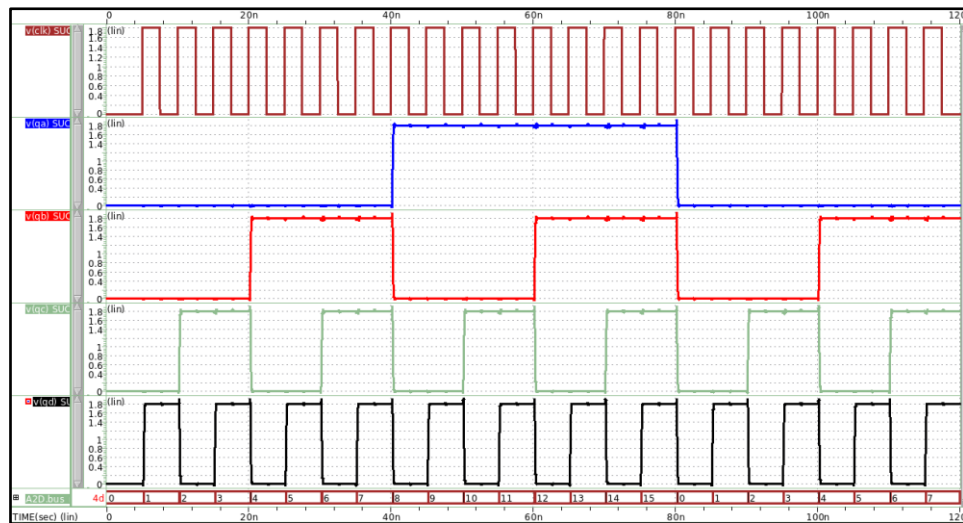


圖 6 4 bits synchronous up counter waveview

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
glitch1_2= 36.6799p targ= 10.2968n trig= 10.2601n
glitch3_4= 36.8311p targ= 20.2979n trig= 20.2611n
glitch5_6= 36.6419p targ= 30.2975n trig= 30.2608n
glitch7_8= 36.9010p targ= 40.2971n trig= 40.2602n
glitch9_10= 36.6806p targ= 50.2969n trig= 50.2602n
glitch11_12= 36.7982p targ= 60.2978n trig= 60.2610n
glitch13_14= 36.6717p targ= 70.2969n trig= 70.2602n
glitch15_0 = 396.3038f targ= 80.2973n trig= 80.2969n
pvdd=-412.4095u from= 0. to= 120.0000n
```

Glitch 皆發生在 odd number to even number 之間，從 truth table 可以解釋此現象，因 1 to 2(0001 → 0010)、3 to 4(0011 → 0100)、5 to 6(0101 → 0110)...等，皆不只一個 bit 轉態，且每個 bit 轉態時間不同，導致 glitch 現象(1 to 2 中間出現 3、3 to 4 中間出現 7...等)。

Glitch and power consumption reducing way

1. Reduce power consumption 的方法：

降低 transistor size。將 transistor size(以 unit inverter 為例)設為

pmos width=0.6 μ m;nmos width=0.3 μ m。模擬後如下：

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
glitch1_2= 47.1119p targ= 10.2755n trig= 10.2284n
glitch3_4= 47.1851p targ= 20.2757n trig= 20.2285n
glitch5_6= 47.1297p targ= 30.2753n trig= 30.2282n
glitch7_8= 47.4101p targ= 40.2759n trig= 40.2285n
glitch9_10= 47.1724p targ= 50.2764n trig= 50.2293n
glitch11_12= 47.3275p targ= 60.2757n trig= 60.2284n
glitch13_14= 47.2000p targ= 70.2754n trig= 70.2282n
glitch15_0= 357.8739f targ= 80.2769n trig= 80.2766n
pvdd=-127.9099u from= 0. to= 120.0000n
```

Power consumption=127.9 μ ;

Power consumption 從原本的 412.4095 μ 降低到 127.9099 μ ，但 glitch 增加了，因 glitch 發生的原因是 current state 轉態時間(falling time)與 next state 轉態時間(rising time)存在 delay。

2. Glitch reduce:

因 glitch 發生的原因是 current state 轉態時間(falling time)與 next state 轉態時間(rising time)存在 delay。故要降低 glitch time 須提高 pull down network 的能力(reduce falling time)，將 nmos width 增加即可做到。我將 XOR gate 的 nmos width=1.25 μ m，其餘不變，模擬結果如下：

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
glitch1_2= 128.7492f targ= 10.3385n trig= 10.3384n
glitch3_4= 586.5219f targ= 20.3387n trig= 20.3382n
glitch5_6= 147.5524f targ= 30.3384n trig= 30.3383n
glitch7_8= 657.6079f targ= 40.3391n trig= 40.3384n
glitch9_10= 324.8772f targ= 50.3388n trig= 50.3385n
glitch11_12= 465.6200f targ= 60.3387n trig= 60.3382n
glitch13_14= 188.5074f targ= 70.3387n trig= 70.3385n
glitch15_0= 668.1028f targ= 80.3390n trig= 80.3383n
pvdd=-168.6429u from= 0. to= 120.0000n
```

Glitch 降至 femto 等級，雖然 power consumption 有略微上升，但仍比最一開始設計時表現還佳。

- (b) Please list the glitch in each number (0 ~ 15) and find the maximum glitch.

Number to number	Glitch Value	Glitch Time
0-1	NA	0s
1-2	3	128.75fs
2-3	NA	0s
3-4	7	586.52fs
4-5	NA	0s
5-6	7	147.55fs
6-7	NA	0s
7-8	15	657.61fs
8-9	NA	0s
9-10	11	324.88fs
10-11	NA	0s
11-12	15	465.62fs
12-13	NA	0s
13-14	15	188.51fs
14-15	NA	0s
16-0	NA	668.1fs
Maximum Glitch		
668.1fs		

- (c) Please measure the power of the counter.


pvdd=-168.6429u from= 0. to= 120.0000n

Power consumption=168.6429μW

2. Please design a 3 bit pseudo-random-bit-sequence (PRBS) generator with Linear Feedback Shift Register (LFSR) with clock frequency CLK = 200MHz, VDD = 1.8V, VSS = 0V. Try to minimize the power consumption of the PRBS generator.
- (a) Please describe how you design the PRBS generator and show the pseudo-random sequence result to prove your design.

PRBS Design

參考講義上 pseudo-random sequence 的電路如下：

 

其 Q[1]、Q[2]、Q[3]會依照下表進行循環：

Table 10.6 LFSR sequence			
Cycle	Q [1]	Q [2]	Q [3] / Y
0	1	1	1
1	0	1	1
2	0	0	1
3	1	0	0
4	0	1	0
5	1	0	1
6	1	1	0
7	1	1	1
repeats forever			

The way to minimize the power


設計 3 bits 的 pseudo random bit sequence 的 mos parameter，原先採用的 mos 大小為 nmos width=1 μ m，pmos width=2 μ m 進行設計，模擬後得到的 power consumption 如下：

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
pvdd=-117.6585u from= 0. to= 120.0000n
```

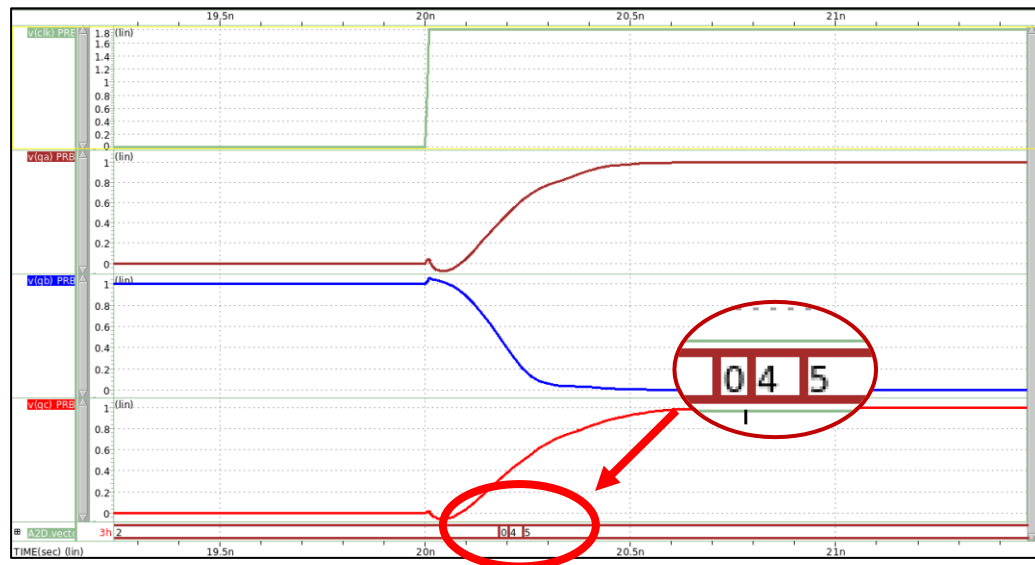1. 方法一:降低 VDD

將 VDD 從 1.8V 降至 1V，模擬結果如下：

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
pvdd= -6.9539u from= 0. to= 120.0000n
```




雖然 power consumption 降低到非常小，但電路的 glitch 更大，超過 80ps，固本題不採用降低 VDD 的方法去降低 power consumption。

將整體 mos size 降低，nmos width=0.25 μ m，pmos width=0.3 μ m，得到的 power consumption 如下：

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
pvdd= -24.0383u from= 0. to= 120.0000n
```

電路功能也可正常運作：

 

結論：

雖然降低 VDD 會得到更好的功耗表現，但也影響電路功能，而調低 mos size 雖然沒有比直接調整 VDD 來的更有成效，但仍可明顯降低 power consumption。

(b) Please measure the power of the PRBS generator.

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
pvdd= -24.0383u from= 0. to= 120.0000n
```

Power consumption=24.0483μW